

# Complex Combinational Logic: Implementation and Design Tradeoffs


# Lecture Goals

---

- Learn some advanced Minispec features that enable implementing large circuits succinctly
  - Parametric functions
  - Type inference and user-defined types
  - Loops and control-flow statements
- Study design tradeoffs in combinational logic by analyzing different adder implementations
 
# Reminder: Shifts


- Fixed-size shifts are cheap
  - Just wires
- What about variable-size shifts?



- Suppose we want to build a shifter that right-shifts a 32-bit value  $x$  by  $n$ , where  $n$  is between 0 and 31
- Naïve approach: Select from 32 different fixed-size shifters using a mux

*Expensive!*

*$n*(n-1)$  2-way 1-bit muxes*

 


# Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by  $n$  using a series of fixed-size shifts by power-of-2 sizes
  - For example, shift by 5 ( $=4+1$ ) can be done with shifts of sizes 4 and 1
  - The bit encoding of  $n$  tells us which shifts are needed: if the  $i^{th}$  bit of  $n$  is 1, then we need to shift by  $2^i$
  - Implementation: A cascade of  $\log_2 n$  muxes that choose between shifting by  $2^i$  and not shifting

*How many 2-way 1-bit muxes?*

$$n * \log_2 n$$

 

# Implementing Large Circuits in Minispec

# Parametric Types

---

- $\text{Bit}\#(n)$ , an  $n$ -bit value, is a **parametric type**
  - $n$  is the **parameter** (an Integer value)
  - Using  $\text{Bit}\#(n)$  requires specifying  $n$  (e.g.,  $\text{Bit}\#(4)$  is a 4-bit value)
- Minispec provides other parametric types, and lets you define your own
  - Parametric types are *generic*
  - They take one or more parameters
  - Parameters must be known at compile-time
  - Specifying the parameters yields a *concrete* type
- Parameters can be Integers or types
  - Example:  $\text{Vector}\#(n, T)$  is an  $n$ -element vector of  $T$ 's (e.g.,  $\text{Vector}\#(4, \text{Bit}\#(8))$  = 4-elem vector of 8-bit values)

# Parametric Functions

---


- Functions have fixed argument and return types
  - Problem 1: Have to write a function for every bit width
  - Problem 2: If we build large functions from smaller ones, have to write many functions! (e.g.,  $\text{rca2} \rightarrow \text{rca4} \rightarrow \text{rca8} \dots$ )
- Parametric functions solve these problems: We can write one *generic* function that covers every case
  - Example:  $\text{rca\#}(n)$ , an  $n$ -bit ripple-carry adder
- A parametric function must be invoked with fixed parameters, which instantiates a *concrete* function
  - Example: Calling  $\text{rca\#}(32)$  instantiates a 32-bit adder

# Example: Parametric Parity

```
function Bit#(1) parity#(Integer n)(Bit#(n) x);  
    return (n == 1)? x : x[n-1] ^ parity#(n-1)(x[n-2:0]);  
endfunction
```

- The parameter  $n$  is used as a variable in the function
- Large circuits implemented by composing smaller ones:  $\text{parity}\#(n)$  invokes  $\text{parity}\#(n-1)$ !
- If another function calls  $\text{parity}\#(3)$ , compiler produces:
 
```
function Bit#(1) parity#(3)(Bit#(3) x);  
    return x[2] ^ parity#(2)(x[1:0]);  
endfunction  
function Bit#(1) parity#(2)(Bit#(2) x);  
    return x[1] ^ parity#(1)(x[0:0]);  
endfunction  
function Bit#(1) parity#(1)(Bit#(1) x);  
    return x;  
endfunction
```






# Integer is a Special Type

Always evaluated by the compiler

---

- Integer values are (positive or negative) numbers with an **unbounded number of bits**
  - Unbounded bits → Cannot be synthesized to hardware
- Integers are guaranteed to be evaluated at compile time, i.e., turned into fixed numbers
  - If the compiler cannot evaluate an Integer expression, it throws an error
- Integer supports the same operations as Bit#(n), (arithmetic, logical, comparisons, etc.)
  - But evaluated by compiler → operations on Integers never produce any hardware

# N-bit Ripple-Carry Adder

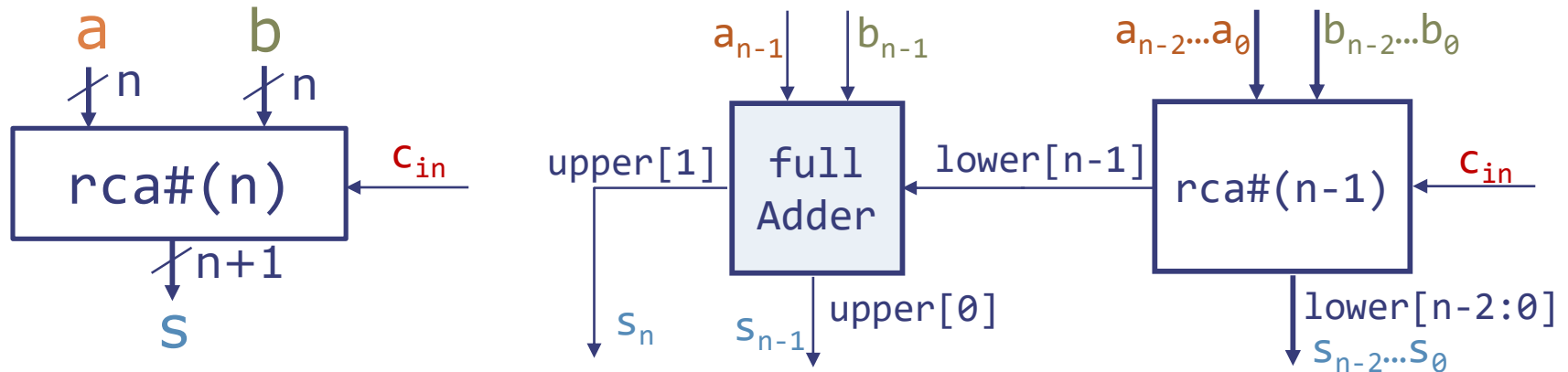

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) lower = rca#(n-1)(a[n-2:0], b[n-2:0], cin);
    Bit#(2) upper = fullAdder(a[n-1], b[n-1], lower[n-1]);
    return {upper, lower[n-2:0]};
endfunction
```

// Base case

```
function Bit#(2) rca#(1)(Bit#(1) a, Bit#(1) b, Bit#(1) cin);
    return fullAdder(a, b, cin);
endfunction
```

# Type Inference

---

- You can omit the type of a variable by declaring it with the `let` keyword
- The compiler infers the variable's type from the type of the expression assigned to the variable

```
Bit#(4) x = 4'b0011;  
let y = x;           // y has type Bit#(4)  
let z = {x, x};      // z has type Bit#(8)  
let w = 2'b11;       // w has type Bit#(2)  
let n = 42;          // n has type Integer
```

# User-Defined Types

---

- **Type synonyms** allow giving a different name to a type
- **Structs** represent a group of member values with different types
- **Enums** represent a set of symbolic constants
- Structs and enums are much clearer than using raw bits!
  - e.g., `Bit#(24) pixel; pixel[15:8]` versus `pixel.green`

```
typedef Bit#(8) Byte;
```

```
typedef struct {  
    Byte red;  
    Byte green;  
    Byte blue;  
} Pixel;
```

```
Pixel p;  
p.red = 255;
```

```
typedef enum {  
    Ready, Busy, Error  
} State;
```

```
State state = Ready;
```

# For Loops



- For loop statements allow compactly expressing a sequence of similar statements

```
Bit#(6) w = 0;  
for (Integer i = 0; i < 6; i = i + 1)  
    w[i] = z[i / 2];
```

- For loops are not like loops in software programming languages!


- Fixed number of iterations**  
(Integer induction variable!)
- Unrolled** at compile time

- Example: The loop above is translated into this sequence:

```
w[0] = z[0];  
w[1] = z[0];  
w[2] = z[1];  
w[3] = z[1];  
w[4] = z[2];  
w[5] = z[2];
```

# N-bit Ripple-Carry Adder with Loop

---

 

```
function Bit#(n+1) rca#(Integer n)(Bit#(n) a, Bit#(n) b, Bit#(1) cin);
    Bit#(n) s = 0;
    Bit#(n+1) c = {0, cin};
    for (Integer i = 0; i < n; i = i + 1) begin
        let x = fullAdder(a[i], b[i], c[i]);
        s[i] = x[0];
        c[i+1] = x[1];
    end
    return {c[n], s};
endfunction
```

# Conditional Statements



- If statements have a syntax similar to software:

```
function Bit#(4) max(Bit#(4) a,      function Bit#(4) max(Bit#(4) a,
                                Bit#(4) b);                                Bit#(4) b);
    Bit#(4) result = b;
    if (a > b) result = a;
    return result;
endfunction                          Bit#(4) result;
                                    if (a > b) result = a;
                                    else result = b;
                                    return result;
                                    endfunction
```

- But they are **implemented very differently** from software programming languages!
  - Translated to muxes, like conditional expressions
  - Each variable assigned within an if statement uses a mux to select the right value (the one assigned in the if branch, else branch, or the previous value)
- Minispec also has case statements (see tutorial)

# Minispec Takeaways

---

- Minispec lets you build circuits with constructs similar to those of software programming languages
- But keep in mind that the implementation of these features is often quite different from software!
  - Parametric functions and types are **instantiated**
  - Functions are **inlined**
  - Conditionals (`?:`, if-else, case) are translated to **multiplexers**, and all their branches are evaluated
  - Loops are **unrolled**
  - What remains is an acyclic graph of gates

Never forget that you're designing hardware




# Design Tradeoffs in Combinational Circuits

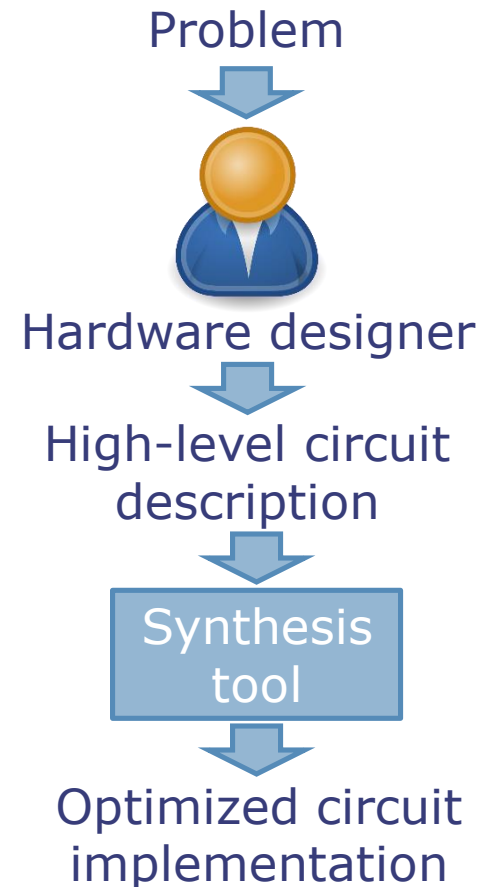
# Algorithmic Tradeoffs in Hardware Design

---

- Each function often allows many implementations with widely different delay, area, and power
- Choosing the right **algorithms** is key to optimizing your design
  - Tools cannot compensate for an inefficient algorithm (in most cases)
  - Just like programming software
- Case study: Building a better adder



# Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001

$$t_{PD} = n * t_{PD,FA} \approx \Theta(n)$$

- $\Theta(n)$  is read "order n" and tells us that the latency of our adder grows **linearly** with the number of bits of the operands

# Asymptotic Analysis

---

- Formally,  $g(n) = \Theta(f(n))$  iff there exist  $C_2 \geq C_1 > 0$  such that for all but *finitely many* integers  $n \geq 0$ ,


$$\underbrace{C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)}$$

$g(n) = O(f(n))$

$\Theta(\dots)$  implies both inequalities;  
 $O(\dots)$  implies only the first.

- Example:  $n^2 + 2n + 3 = \Theta(n^2)$  (read “is of order  $n^2$ ”) since  $2n^2 > n^2 + 2n + 3 > n^2$  except for a few small integers
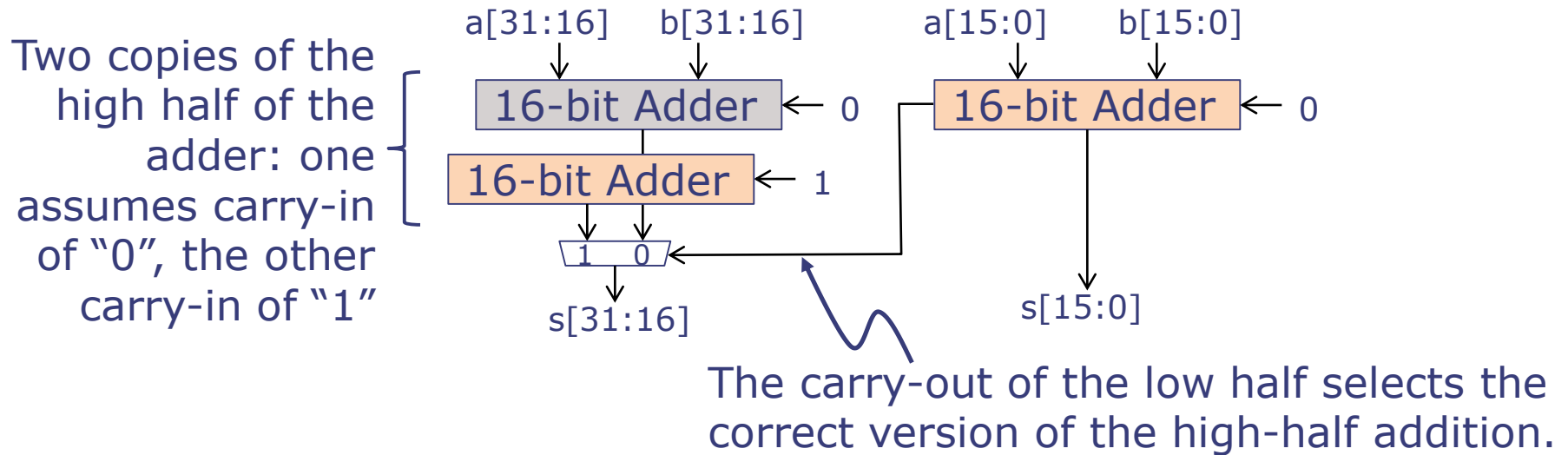
# Carry-Select Adder Trades Area for Speed




- Propagation delay:  $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$ 
  - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder
  - If we apply the same strategy recursively (build each 16-bit adder from 8-bit carry-select adders, etc.),  $t_{PD,n} = \Theta(\log n)$

*Drawbacks? Consumes much more area than ripple-carry adder  
Wide mux adds significant delay (lab 4)*
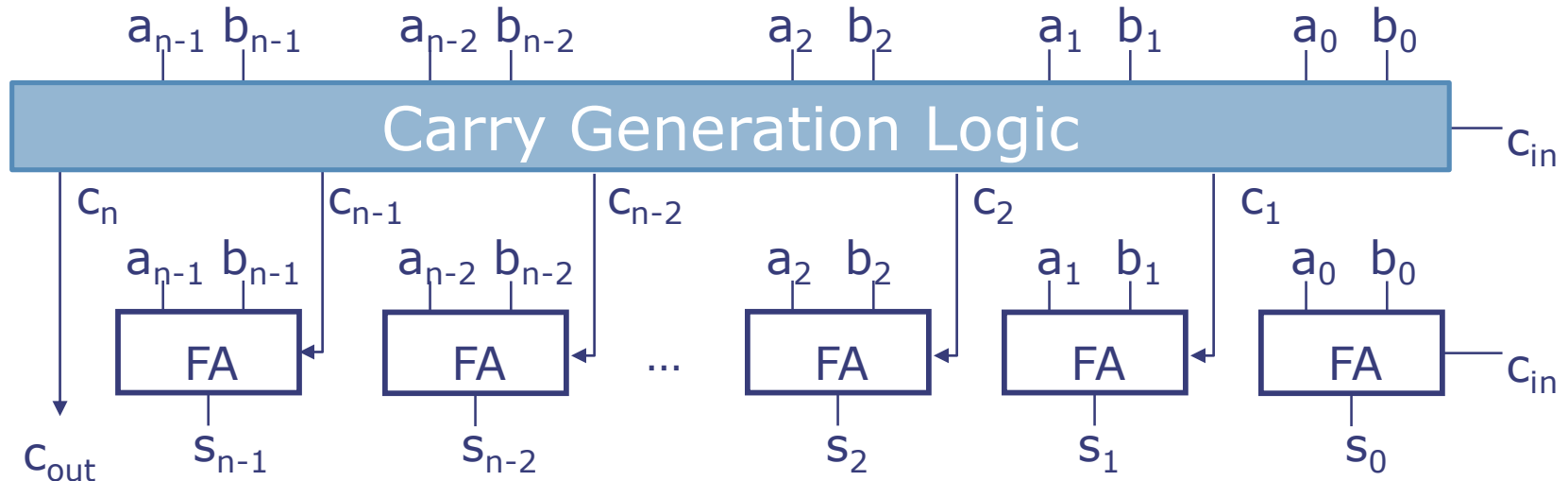
# Carry-Lookahead Adders (CLAs)


- CLAs compute all carry bits in  $\Theta(\log n)$  delay



- Key idea: Transform chain of carry computations into a tree
  - Transforming a chain of associative operations (e.g., AND, OR, XOR) into a tree is easy
  - But how to do this with carries?

# Carry Generation and Propagation

---

 


$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = ab + ac_{in} + bc_{in}$$

- We can rewrite  $c_{out} = ab + (a+b)c_{in}$   
as  $c_{out} = g + pc_{in}$   
with  $g = ab$  (generate)  
and  $p = a+b$  (propagate)
  - $g=1 \rightarrow c_{out} = 1$  (FA generates a carry)
  - $p=1$  (and  $g=0$ )  $\rightarrow c_{out} = c_{in}$  (FA propagates carry)

Note  $p$  and  $g$  don't depend upon  $c_{in}$

 
# Generate and Propagate Compose Hierarchically!



$$C_{out} = g + p \cdot C_{in}$$


$$\text{where } g = a \cdot b \text{ and } p = a + b$$

 - Consider a 2-bit ripple-carry adder. Let's derive  $c_2$  as a function of  $c_0$  and the individual  $g$ 's and  $p$ 's



$$\begin{aligned} c_2 &= g_1 + p_1 c_1 = g_1 + p_1 (g_0 + p_0 c_0) \\ &= \underbrace{g_1 + p_1 g_0}_{g_{10}} + \underbrace{p_1 p_0}_{p_{10}} c_0 \end{aligned}$$

- What about a 4-bit adder?

 

$$g_{10} = g_1 + p_1 g_0$$

$$p_{10} = p_1 p_0$$

$$g_{32} = g_3 + p_3 g_2$$

$$p_{32} = p_3 p_2$$

$$g_{30} = g_{32} + p_{32} g_{10}$$

$$p_{30} = p_{32} p_{10}$$

$$c_4 = g_{30} + p_{30} c_0$$




# CLA Building Blocks

---


- Step 1: Generate individual  $g$  &  $p$  signals



 - Step 2: Combine adjacent  $g$  &  $p$  signals




- Step 3: Generate individual carries

 

There are many CLA variants. Let's derive the Brent-Kung CLA.


# Generating and Combining gp's

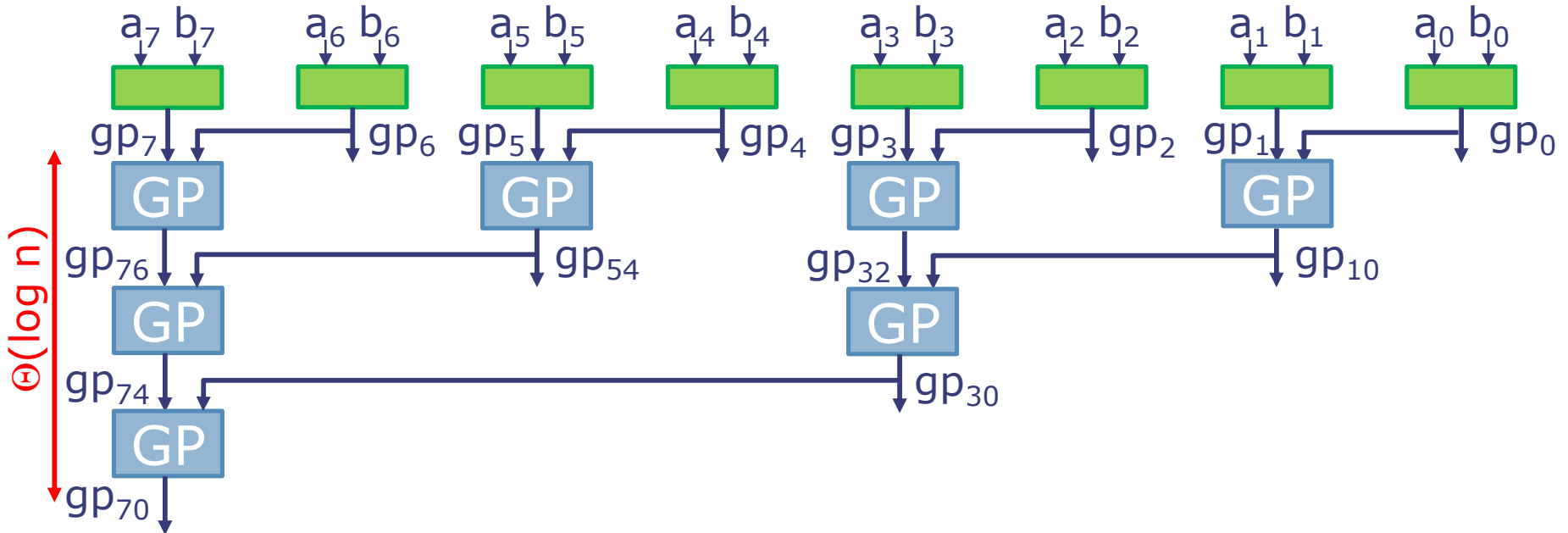

*How does delay grow  
with number of bits?*

$\Theta(\log n)$

# Generating the Carries

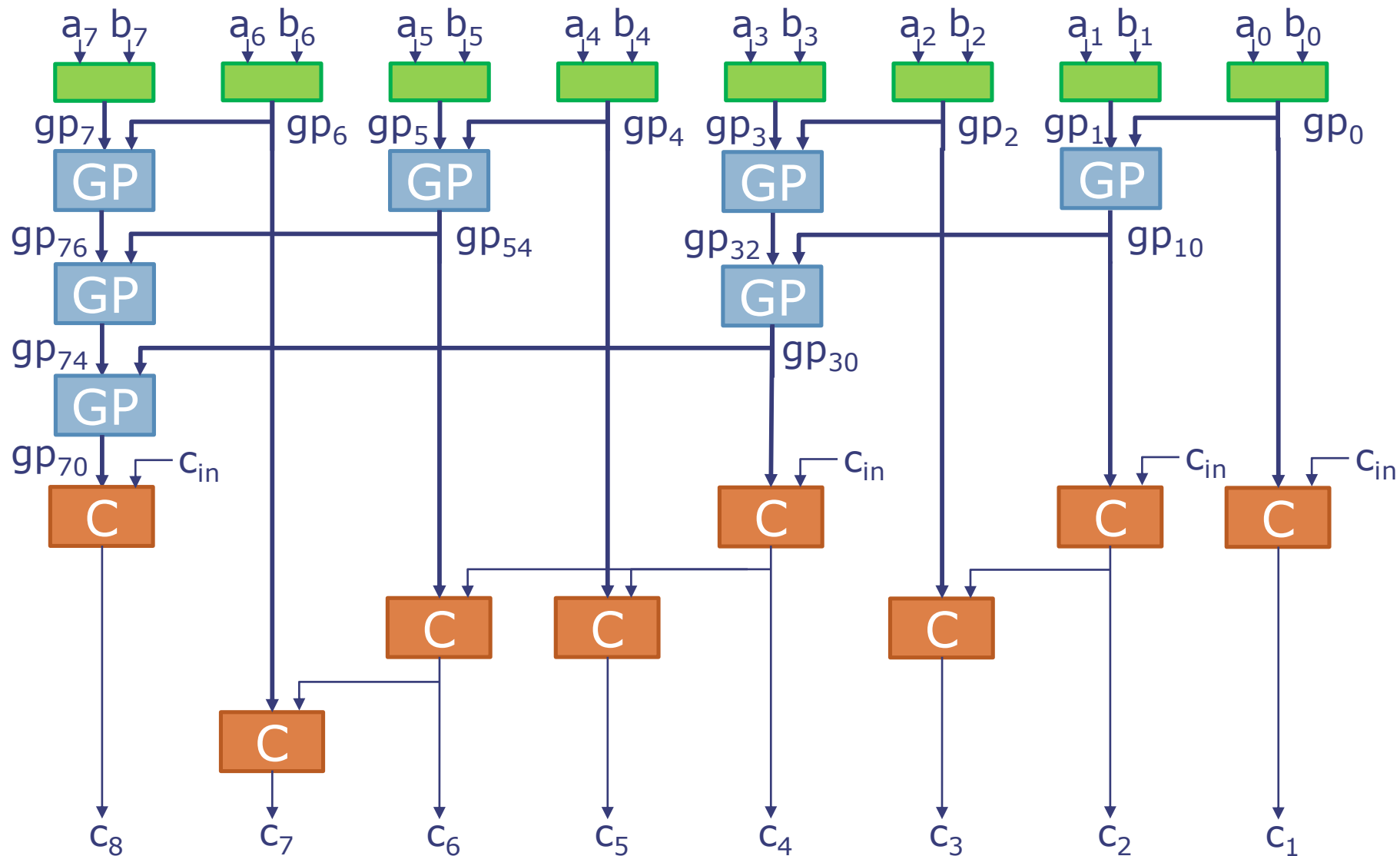

# Carry-Lookahead Adder Takeaways

---

- There are many CLA designs
  - We've seen a Brent-Kung CLA
  - Several other types (e.g., Kogge-Stone)
  - Different variants for each type, e.g., using higher-radix trees to reduce depth
- This technique is useful beyond adders: computes any one-dimensional binary recurrence in  $\Theta(\log n)$  delay
  - e.g., comparators, priority encoders, etc.

# Summary

---

- Parametric functions let us write a generic description of a function that is then instantiated on demand
- Use for loops and if-else statements with care: their similarity to software can be confusing and they can lead to poor circuits
- Choosing the right algorithms is crucial to design good digital circuits—tools can only do so much!
- Carry-lookahead adders perform  $\Theta(\log n)$  addition with modest area cost. This technique can be used to optimize a broad class of circuits

# Thank you!

Next lecture: CMOS