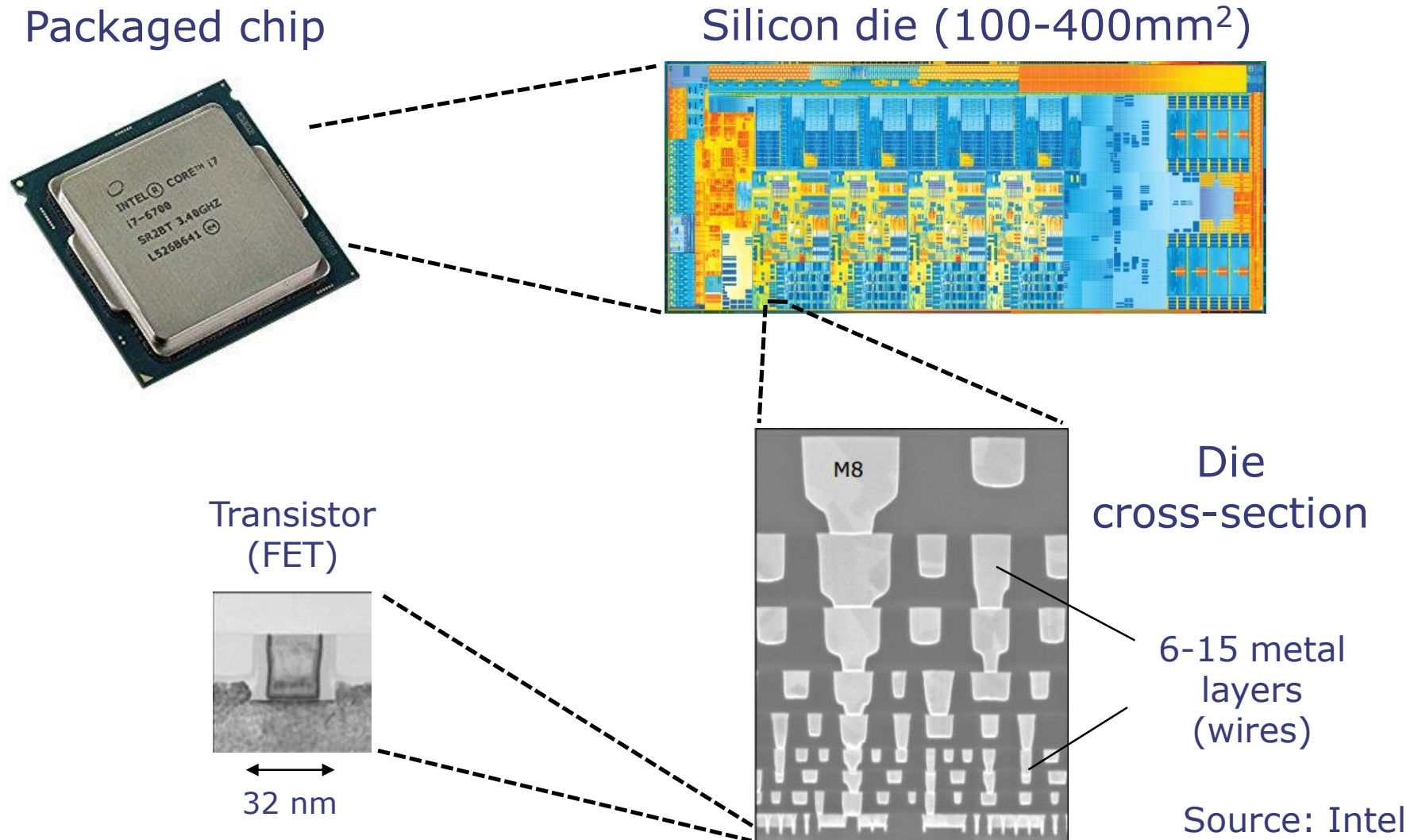



CMOS Technology

A Deep Dive Into a Chip




Field-Effect Transistors (FETs)

 - Nearly all digital systems are built using field-effect transistors, which are **voltage-controlled switches**
- FETs come in two varieties: nFET and pFET




 
A high voltage at gate
creates conducting path
between source and drain



A low voltage at gate
creates conducting path
between source and drain

Labeling Source and Drain

  
- There is no physical difference between source and drain, called the **diffusion terminals**
- By convention, we label diffusion terminals as source or drain depending on their voltages:
 - On nFETs, source = diffusion terminal at lower voltage
 - On pFETs, source = diffusion terminal at higher voltage



- This convention lets us define the behavior of FETs using the voltage between gate and source


FET Switching Model

 - FETs have a **threshold voltage** V_{TH}
- nFET is ON if the voltage between **gate** and **source** V_{GS} exceeds V_{TH} , OFF otherwise
- pFET is ON if the voltage between **source** and **gate** V_{SG} exceeds V_{TH} , OFF otherwise




- This is a very simplified model, but it is sufficient to build logic gates

What Does This Circuit Compute?

 



CMOS inverter

 

Assume $V_{TH} < V_{DD}/2$

$V_{IN} < V_{TH}$

$V_{IN} > V_{DD} - V_{TH}$

  


| IN | OUT |
|----|-----|
| 0 | 1 |
| 1 | 0 |

Note on Terminology


- MOSFETs (metal-oxide-semiconductor field-effect transistors) are the most common type of FET
- nFET and pFET are sometimes abbreviated as nMOS and pMOS
- CMOS stands for complementary MOS

What Does This Circuit Compute?

 

| A | B | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


CMOS NAND gate

 

CMOS Logic

- CMOS gates have **complementary** pullup and pulldown networks, i.e., the pullup is on where the pulldown is off and viceversa


| pullup | pulldown | F(inputs) |
|-----------|-----------|-------------------|
| on | off | driven "1" |
| off | on | driven "0" |
| on | on | driven "X" |
| off | off | no connection |

 


- CMOS uses pFETs to implement the pullup network and nFETs to implement the pulldown network

Some Questionable Gates

 
- What can go wrong with the following gates?



 $A=0$ $B=1$ or $A=1$ $B=0$
connect supply and ground




 pFET doesn't pull down
 V_{OUT} below V_{TH}
nFET doesn't pull up
 V_{OUT} above $V_{DD} - V_{TH}$




- CMOS Rule #1: Complementary pullup and pulldown networks
- CMOS Rule #2: pFETs in pullup, nFETs in pulldown


CMOS Complements

 


conducts when A is high

 


conducts when A is low: \bar{A}

 

 
conducts when A is high
and B is high: $A \cdot B$



 conducts when A is low
or B is low: $\bar{A} + \bar{B} = \overline{A \cdot B}$



 conducts when A is high
or B is high: $A + B$



conducts when A is low
and B is low: $\bar{A} \cdot \bar{B} = \overline{A + B}$

General CMOS Gate Recipe

Step 1. Derive the pullup network that does what you want, e.g.,

$$F = \overline{A} + \overline{B} \times \overline{C}$$




(Determine what combination of inputs generates a high output)

Step 2. Derive complementary pulldown network: replace pFETs with nFETs, series subnets with parallel subnets, and parallel subnets with series subnets

Step 3. Combine pFET pullup network from Step 1 with nFET pulldown network from Step 2 to form the CMOS gate.

Can CMOS gates implement arbitrary functions?

No

   

CMOS Gates are Inverting

- In a CMOS gate, rising inputs ($0 \rightarrow 1$) lead to falling outputs ($1 \rightarrow 0$) and viceversa
- On a rising input,
 - nFETs go OFF \rightarrow ON, so pulldown may connect output to ground
 - pFETs go ON \rightarrow OFF, so pullup may disconnect output from V_{DD}
 - Output either stays the same or falls
- Corollary: Cannot build non-inverting logic using a single CMOS gate
 - Example: AND


| A | B | A·B |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

rising input rising output

Analyzing the Delay, Area, and Power of CMOS Gates


*NOTE: Demystification,
will not be on the quiz*

MOSFET Physical Structure

 


MOSFET Electrical View

 With $V_{GS} < V_{TH}$, almost no current flows between source and drain




 As V_{GS} reaches V_{TH} , a channel forms between source and drain



The shape of the channel (and its resistance) also depends on the voltage at the drain. But a low-resistance channel will exist while $V_{GS} > V_{TH}$




FET *First-Order* Electrical Model

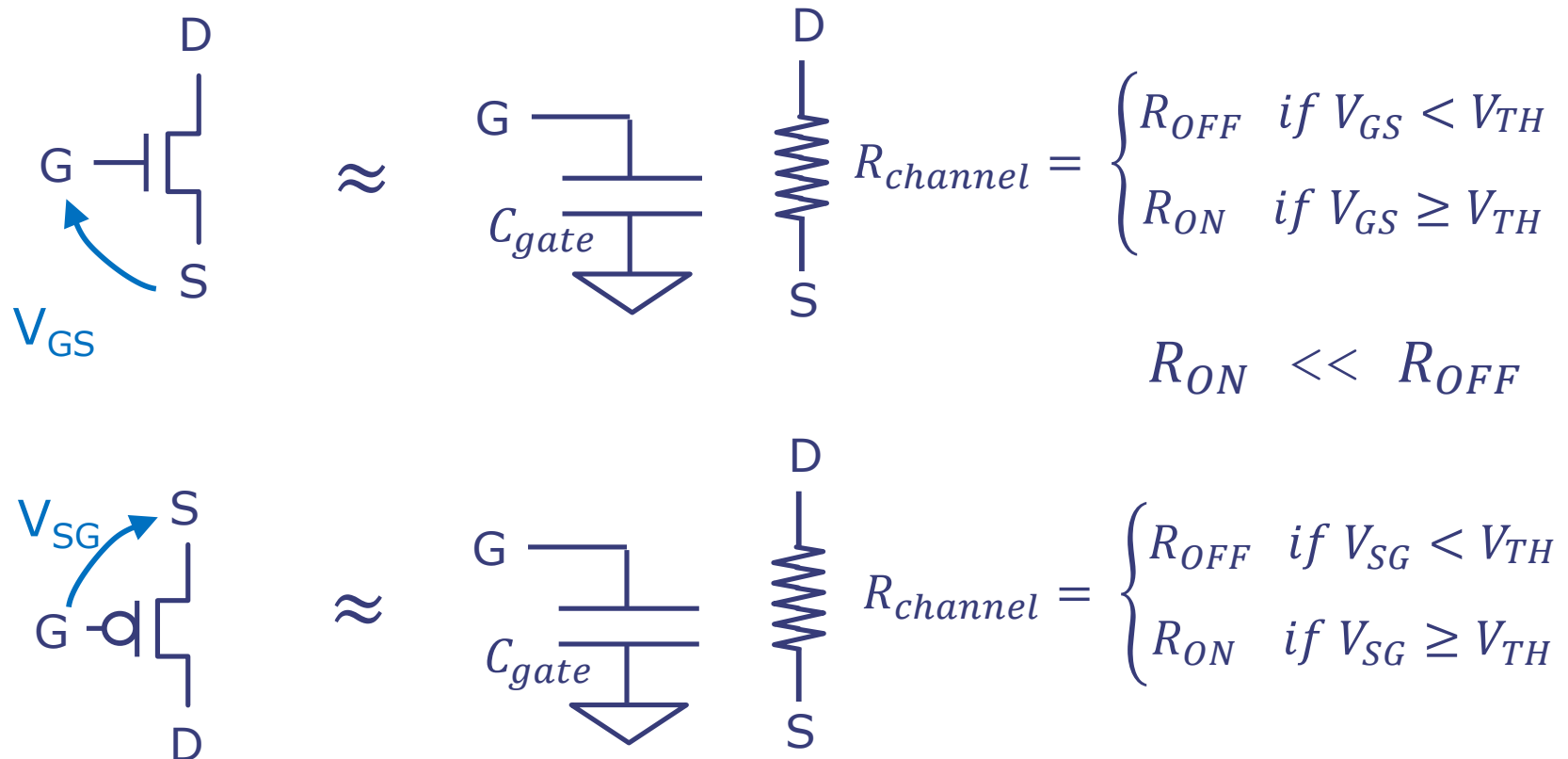

- Simplest possible model that lets us reason about delay, area, and power. Not very accurate!

CMOS Gate Delay

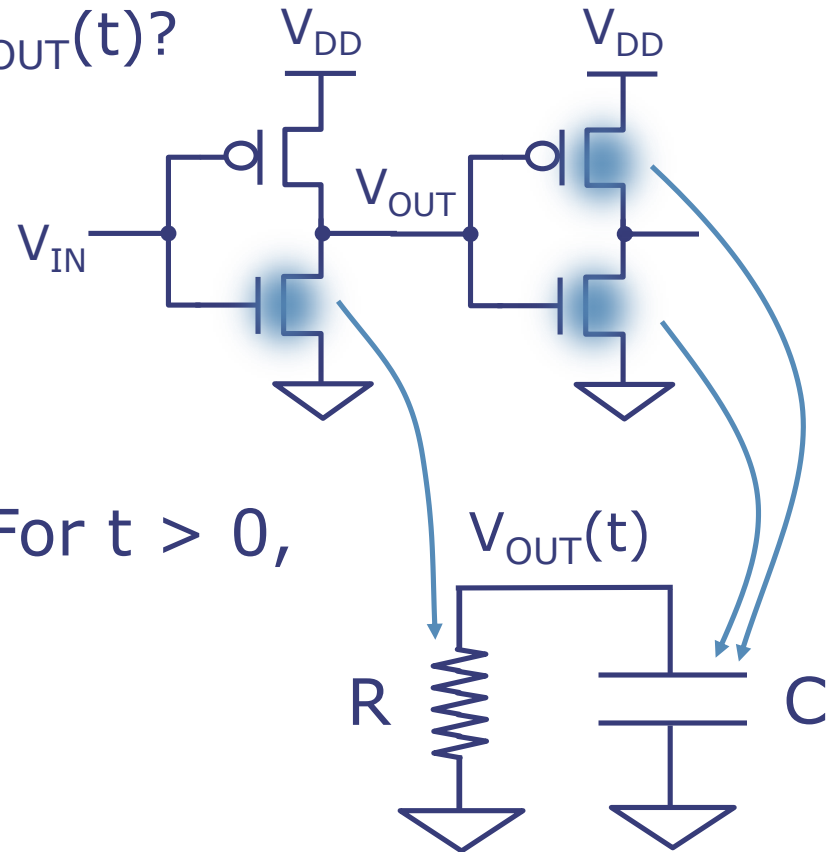  
Consider the following circuit.
Given $V_{IN}(t)$, can you derive $V_{OUT}(t)$?



$$V_{OUT}(t) = V_{OUT}(0)e^{-t/RC}$$

Propagation Delay

 
Propagation delay (t_{pD}): Upper bound on the delay from **valid inputs** to **valid outputs**.





To minimize t_{pD} , must keep resistances and capacitances low

Contamination Delay

 Contamination delay (t_{CD}): Lower bound on the delay from any **invalid input** to an **invalid output**



MOSFET Sizing

  

How do C_{gate} and $R_{channel}$ change with L and W ?


$$C_{gate} \propto L \cdot W$$

$$R_{channel} \propto L/W$$

- CMOS gates use MOSFETs with smallest possible L and choose W to set performance
 - Wider FETs drive more current (lower R), but their gates are harder to drive (higher C) and they take more area


Standard Cell Libraries

 - A standard cell library provides implementations of common gates (NAND, NOR, XOR, etc.) for a specific implementation technology
- Each gate includes
 - Electrical parameters (e.g., R_s and C_s)
 - Physical layout
- Synthesis tools use gates from the standard library instead of sizing and placing individual transistors




Wide (High-Fanin) Gates

 Most standard cell libraries include 2-, 3- and 4-input devices:



But for a large number of inputs, the series connections of too many MOSFETs can lead to very large effective R_{pulldown} or R_{pullup} . Instead, use trees of smaller devices...

Example:
8-input
NAND

 

How does t_{pD} grow with the number of inputs N ?

If we use a single CMOS gate, $t_{pD} \propto N$

If we use a tree of gates, $t_{pD} \propto \log(N)$

CMOS Power Dissipation

- Total power dissipation: $P = P_{dynamic} + P_{static}$
- Dynamic power: Caused by $0 \leftrightarrow 1$ transitions of nodes in the circuit
 - Charging/discharging each capacitor consumes $\frac{1}{2}CV_{DD}^2$ energy
 - If on average C_S capacitance across the chip switches each cycle, and there are f_{CLK} cycles per second

$$P_{dynamic} = \frac{1}{2}C_S V_{DD}^2 f_{CLK}$$

- Static power: Caused by
 - Subthreshold leakage: Even when the FET is off, a very small current flows from source to drain ($R_{OFF} < \infty$)
 - Tunneling current: Gate and channel are separated by a very thin ($< 1\text{nm}$) dielectric, so some electrons tunnel through

$$P_{static} = I_{static} V_{DD}$$

- Static power is typically 10-30% of total power

Summary

- FETs behave as voltage-controlled switches
- CMOS gates:
 - Use complementary pullup and pulldown networks
 - Use pFETs in pullup, nFETs in pulldown network
- CMOS gates are inverting (rising inputs can only cause falling outputs, and viceversa)

Thank you!

Next lecture:
Sequential logic