

# Introduction to Pipelining

## **Reminders:**

Quiz 1 tonight! 7:30-9:30PM  
A-K in 32-123, L-Z in 26-100


Makeup on Monday, 3-5PM in 34-101  
Accommodations on Monday, 3-6PM in 34-101

# Performance Measures

---

- Two metrics of interest when designing a system:
  1. Latency: The *delay* from when an input enters the system until its associated output is produced
  2. Throughput: The *rate* at which inputs or outputs are processed
- The metric to prioritize depends on the application
  - *Airbag deployment system?* Latency
  - *General-purpose processor?* Throughput  
(maximize instructions/second)

# Performance of Combinational Logic

 


For combinational logic:

$$\text{latency} = t_{PD}$$

$$\text{throughput} = 1/t_{PD}$$

 
We can't get the answer any faster, but are we making effective use of our hardware at all times?



F & G are "idle", just holding their outputs stable while H performs its computation

# Pipelined Circuits

Use registers to hold H's input stable!

 


Now F & G can be working on input  $X_{i+1}$  while H is performing its computation on  $X_i$ . We've created a 2-stage *pipeline*: if we have a valid input X during clock cycle j, P(X) is valid during clock cycle j+2.

Suppose F, G, H have propagation delays of 15, 20, 25 ns and we are using ideal registers ( $t_{PD} = 0$ ,  $t_{SETUP} = 0$ ):

	<u>latency</u>	<u>throughput</u>
unpipelined	45	1/45
2-stage pipeline	<u>50</u>	<u>1/25</u>
	worse	better!

# Pipeline Diagrams

 

The results associated with a particular set of input data moves *diagonally* through the diagram, progressing through one pipeline stage each clock cycle.

# Pipeline Conventions

---

## Definition:

A well-formed *K-Stage Pipeline* (“K-pipeline”) is an acyclic circuit having exactly K registers on *every* path from an input to an output.

A combinational circuit is thus a 0-stage pipeline.

## Composition convention:

Every pipeline stage, hence every K-Stage pipeline, has a register on its *output* (not on its input).


## Clock period:

The clock must have a period  $t_{\text{CLK}}$  sufficient to cover the longest register to register propagation delay plus setup time.

$$\begin{aligned} \text{K-pipeline latency } L &= K * t_{\text{CLK}} \\ \text{K-pipeline throughput } T &= 1 / t_{\text{CLK}} \end{aligned}$$

# Ill-Formed Pipelines

Consider a BAD job of pipelining:

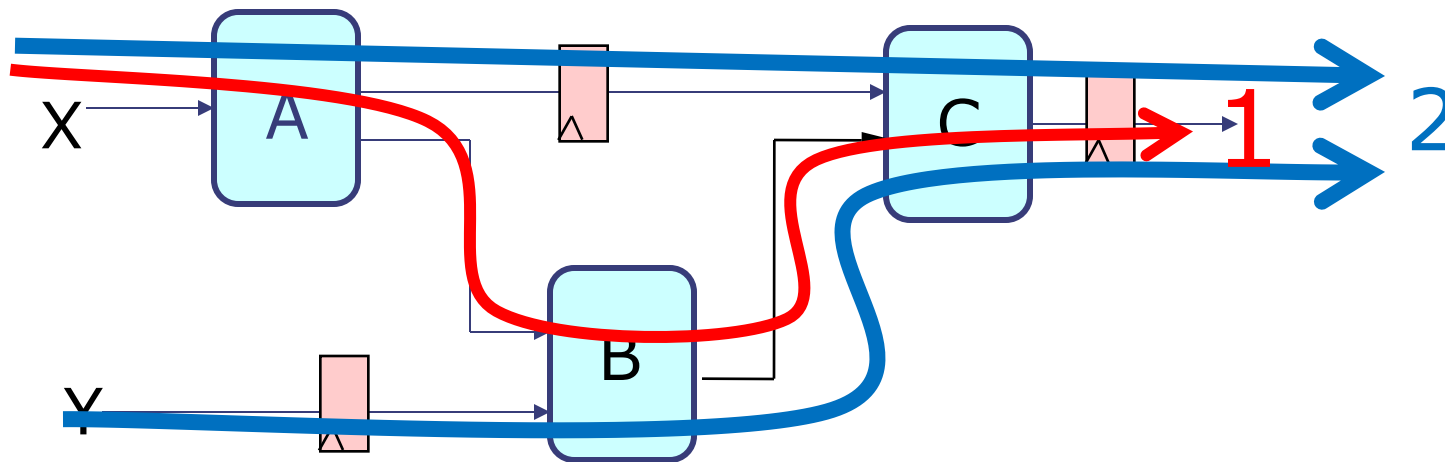

For what value of K is the following circuit a K-Pipeline? *none*

Problem:

*Successive inputs get mixed:* e.g.,  $B(A(X_{i+1}), Y_i)$ .  
This happens because some paths from inputs to outputs have 2 registers, and some have only 1!

*This can't happen in a well-formed K pipeline!*

# A Pipelining Methodology

## Step 1:

Draw a line that crosses every output in the circuit, and mark the endpoints as terminal points.


## Step 2:

Continue to draw new lines between the terminal points across various circuit connections, ensuring that every connection crosses each line in the same direction. These lines demarcate *pipeline stages*.

Adding a pipeline register at every point where a separating line crosses a connection will always generate a valid pipeline.

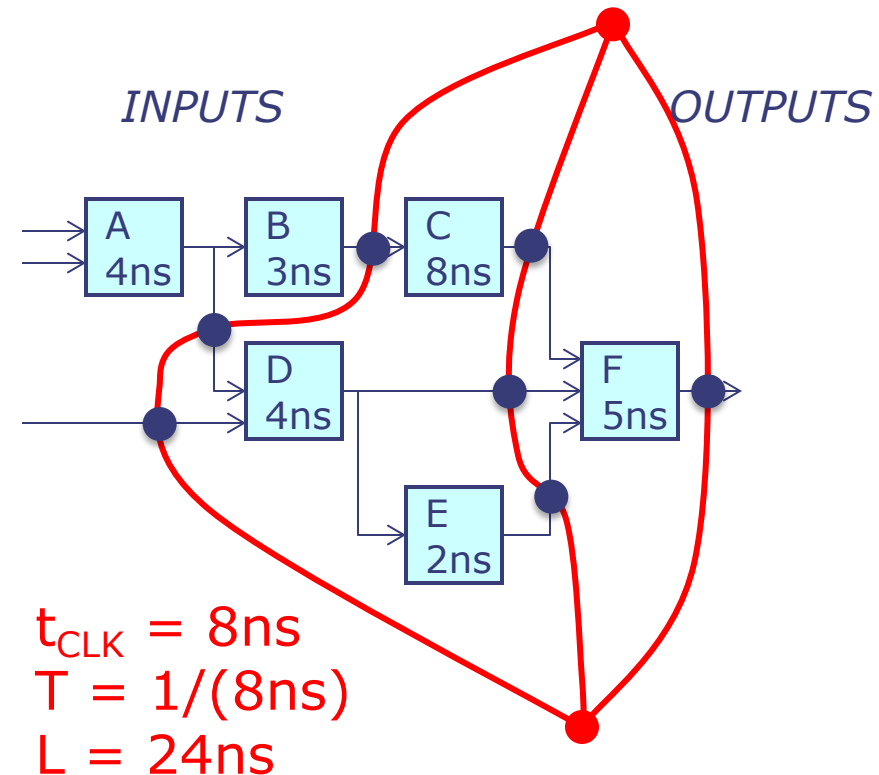
## Strategy:

Focus your attention on placing pipelining registers around the slowest circuit elements (*bottlenecks*).





# Pipeline Example

 


## OBSERVATIONS:

- 1-pipeline improves neither L nor T.
- T improved by breaking long combinational paths, allowing faster clock.
- Too many stages cost L, don't improve T.
- Back-to-back registers are sometimes needed to keep pipeline well-formed.

	LATENCY	THROUGHPUT
0-pipe:	4	1/4
1-pipe:	4	1/4
2-pipe:	4	1/2
3-pipe:	6	1/2

# Pipelined Components

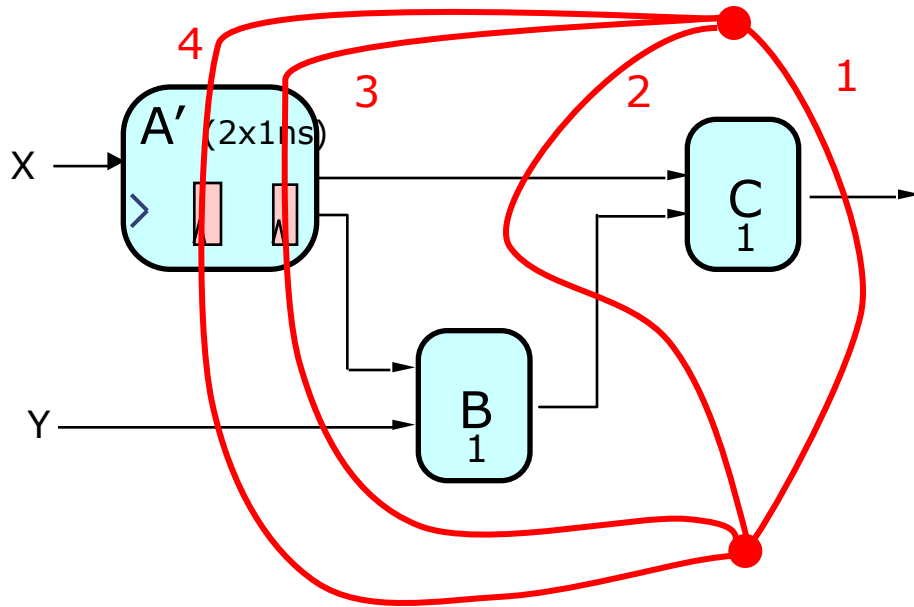


4-stage pipeline, throughput=1

Pipelined systems can be hierarchical:

- Replacing a slow combinational component with a  $k$ -pipe version may let us decrease the clock period
- Must account for new pipeline stages in our plan
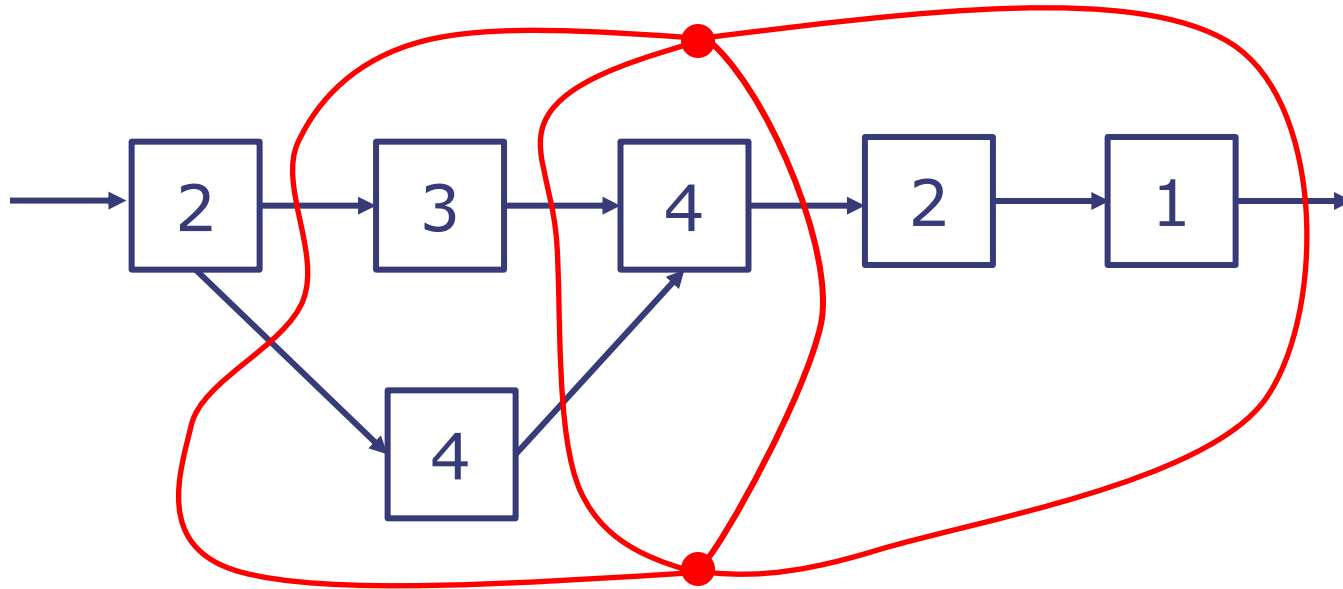
# Sample Pipelining Problem

- Pipeline the following circuit for maximum throughput while minimizing latency. The number in each module is the module's latency.



- What is the latency and throughput of your pipelined circuit?

$$\begin{aligned}t_{\text{CLK}} &= 4 \\T &= 1/(4) \\L &= 4*4 = 16\end{aligned}$$

# Design Tradeoffs

## Introduction:

### Multiplier Case Study

# Multiplication by repeated addition

b Multiplicand 1101 (13)  
a Multiplier \* 1011 (11)

tp  
m0 + 0000  
+ 1101  
tp  
m1 + 01101  
+ 1101  
tp  
m2 + 100111  
+ 0000  
tp  
m3 + 0100111  
+ 1101  
tp 10001111 (143)

At each step we add either 1101 or 0 to the result depending upon a bit in the multiplier

$$m_i = (a[i] == 0) ? 0 : b;$$

We also shift the result by one position at every step

Notice, the first addition is unnecessary because it simply yields m0


Also note that these are unsigned binary numbers.

# Multiplication by repeated addition circuit

b Multiplicand 1101 (13)  
a Multiplier \* 1011 (11)

tp	0000	
m0	+ 1101	
tp	01101	
m1	+ 1101	
tp	100111	
m2	+ 0000	
tp	0100111	
m3	+ 1101	
tp	10001111	(143)

$m_i = (a[i] == 0) ? 0 : b;$

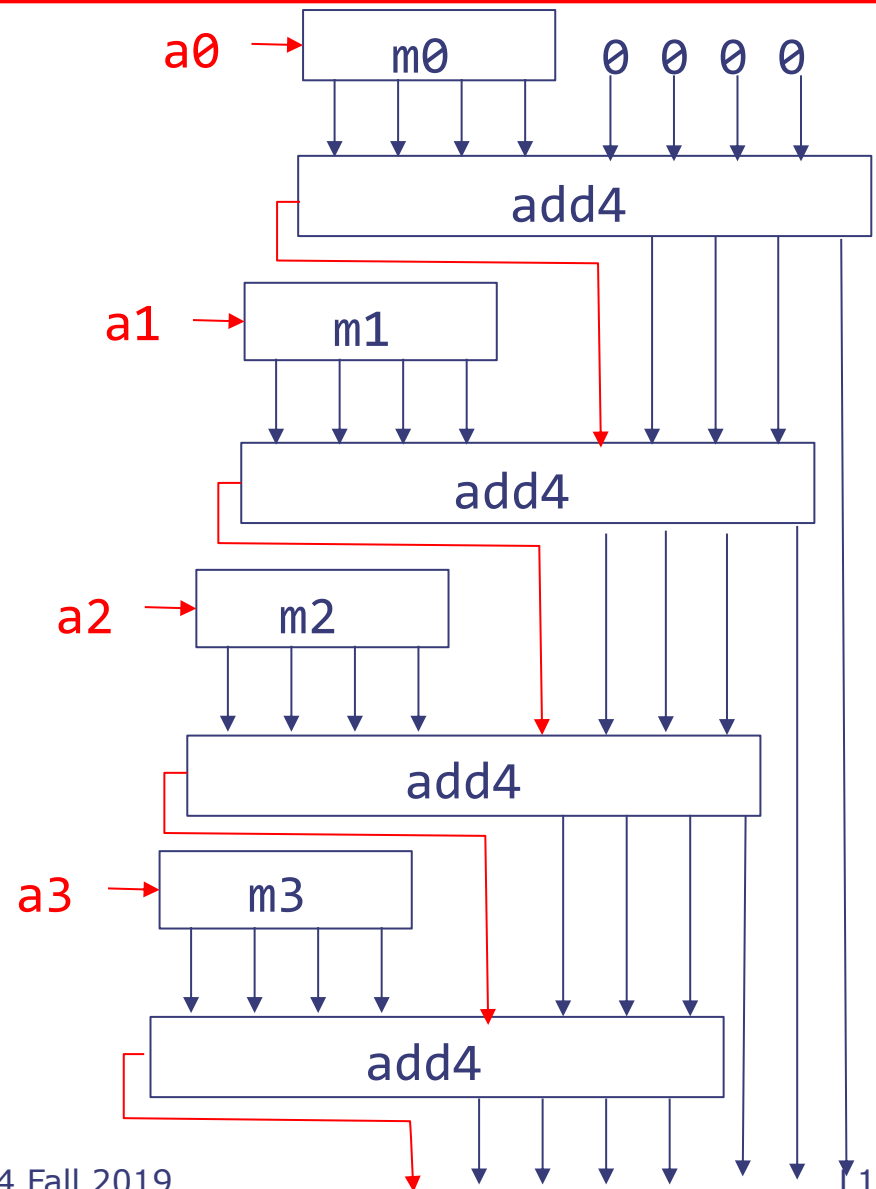

# Implementation of $m_i$

The “Binary”  
Multiplication  
Table

*	0	1
0	0	0
1	0	1

= AND

$$m_i = (a[i] == 0) ? 0 : b;$$

$$\begin{array}{rcccc}
 & B_3 & B_2 & B_1 & B_0 \\
 \times & A_3 & A_2 & A_1 & A_0 \\
 \hline
 BA_i \text{ called a “partial product”} \longrightarrow & B_3A_0 & B_2A_0 & B_1A_0 & B_0A_0 & m0 \\
 & B_3A_1 & B_2A_1 & B_1A_1 & B_0A_1 & m1 \\
 & B_3A_2 & B_2A_2 & B_1A_2 & B_0A_2 & m2 \\
 + & B_3A_3 & B_2A_3 & B_1A_3 & B_0A_3 & m3 \\
 \hline
 \end{array}$$

Multiplying N-digit number by M-digit number gives (N+M)-digit result

Easy part: forming partial products (bunch of AND gates)


Hard part: adding M N-bit partial products
 
# Combinational Multiplier Redrawn




$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$



$$s = a \oplus b$$


$$c_{out} = a \cdot b$$

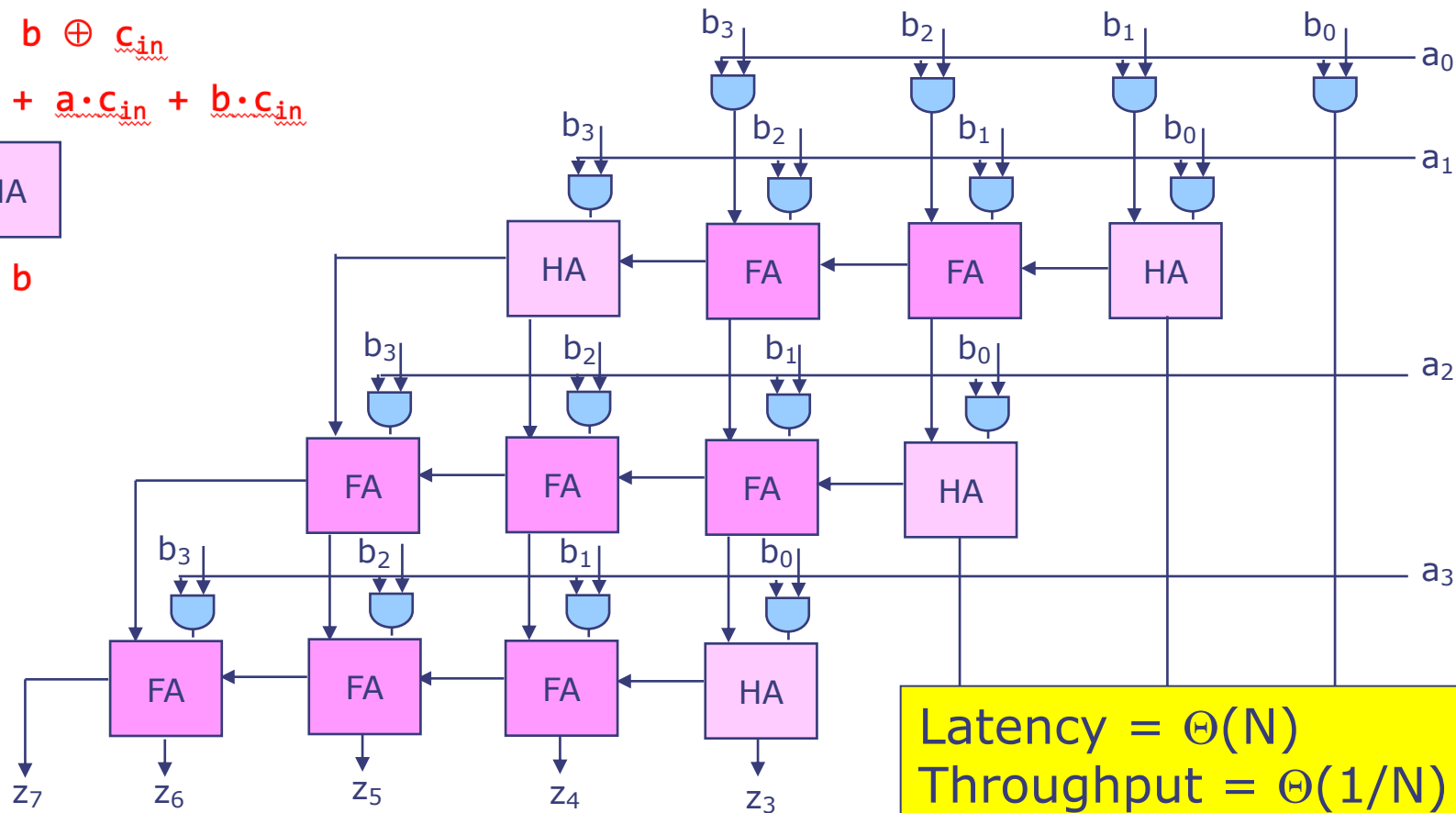

Latency =  $\Theta(N)$   
Throughput =  $\Theta(1/N)$   
Area =  $\Theta(N^2)$



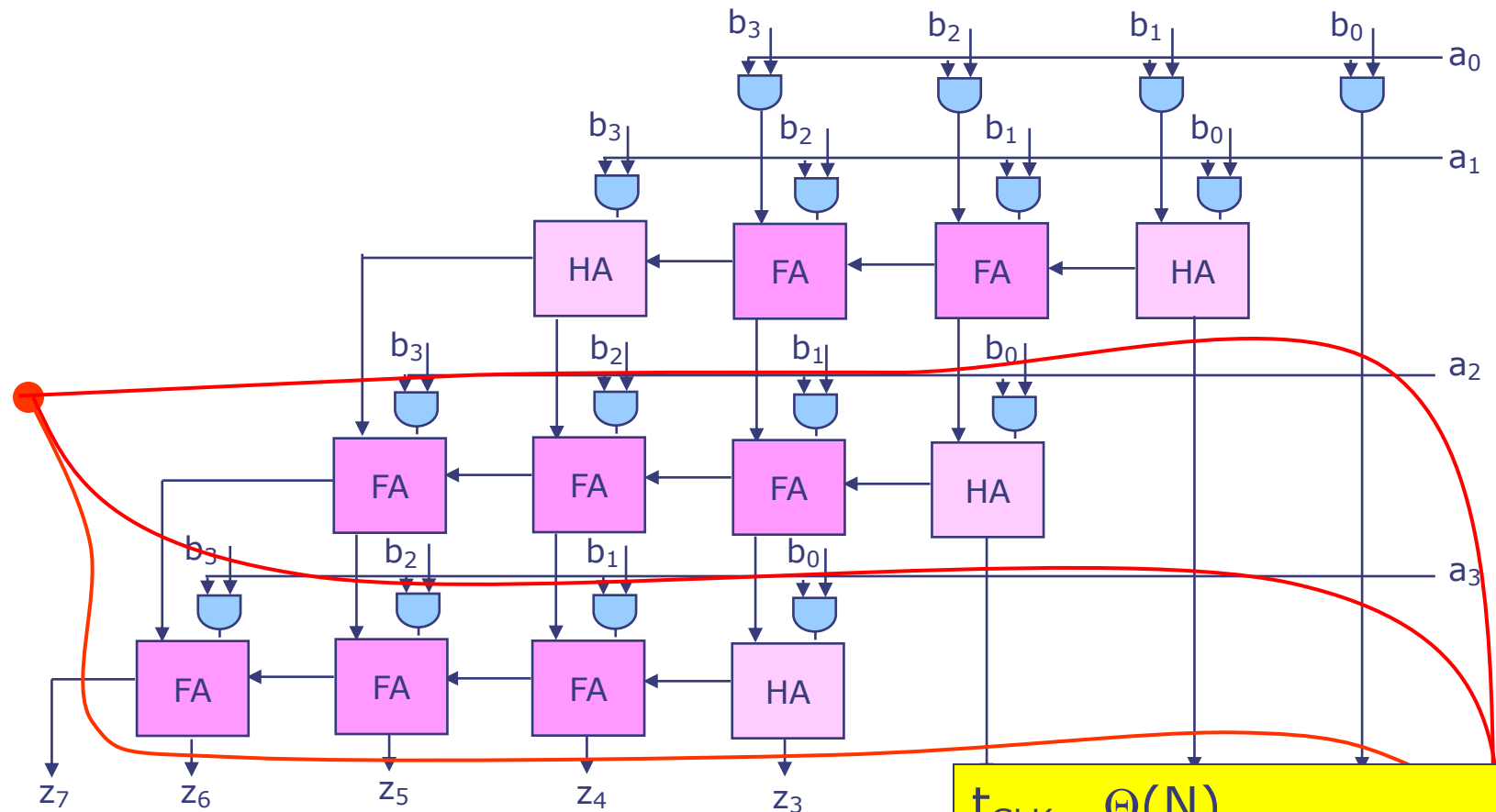
# Increase Throughput with Pipelining - First Attempt



Need to break carry chain

$t_{\text{CLK}} = \Theta(N)$   
# stages =  $\Theta(N)$   
Latency =  $\Theta(N^2)$   
Throughput =  $\Theta(1/N)$


# Increase Throughput with Pipelining

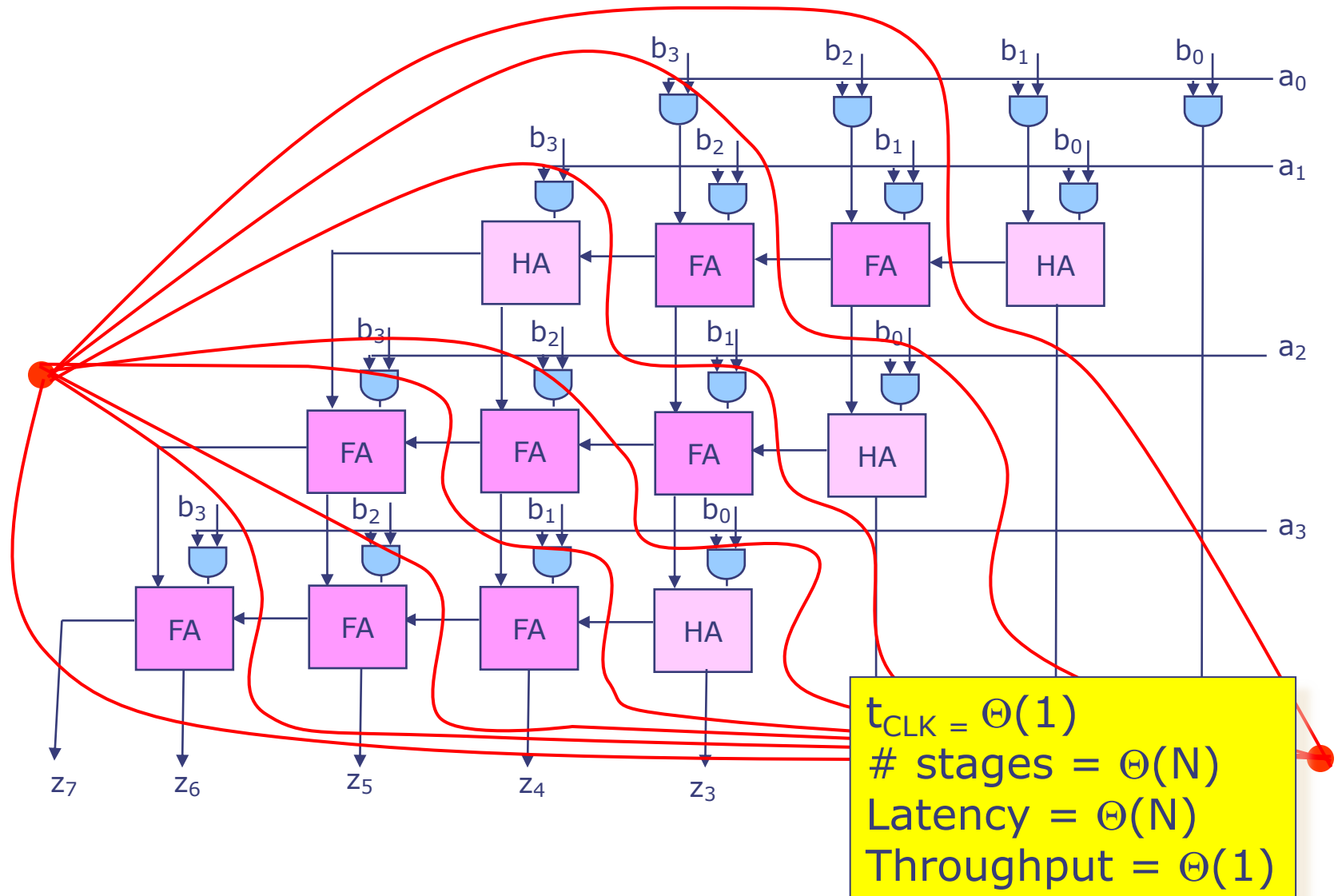

# Folded Multiplier
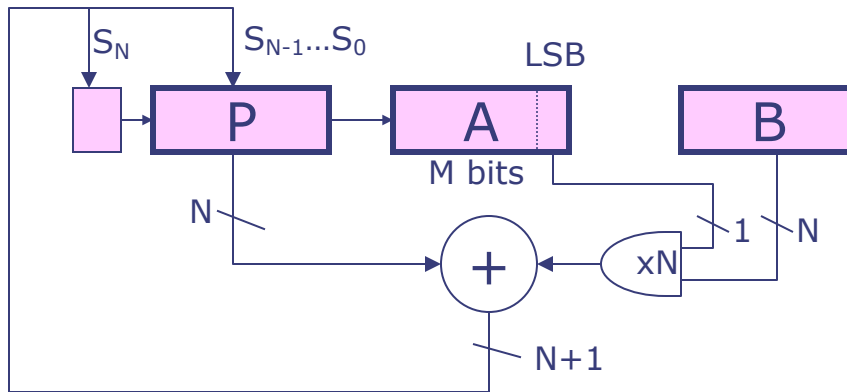
## Reduce Area With Sequential Logic

Assume the multiplicand (B) has N bits and the multiplier (A) has M bits. If we only want to invest in a single N-bit adder, we can process adds sequentially using the same adder M times. **Tradeoff increased latency for reduced area.**



Init:  $P \leftarrow 0$ , load A&B

Repeat M times {  
 $P \leftarrow P + (A_{\text{LSB}} == 1 ? B : 0)$   
 shift  $S_N, P, A$  right one bit  
}

Done: (N+M)-bit result in P,A

Using Ripple Carry Adder

$t_{\text{CLK}} = \Theta(N)$

# stages =  $\Theta(N)$

Latency =  $\Theta(N^2)$

Throughput =  $\Theta(1/N^2)$

Area =  $\Theta(N)$

Using Diagonal Partial Products

$t_{\text{CLK}} = \Theta(1)$

# stages =  $\Theta(N)$


Latency =  $\Theta(N)$

Throughput =  $\Theta(1/N)$


Area =  $\Theta(N)$
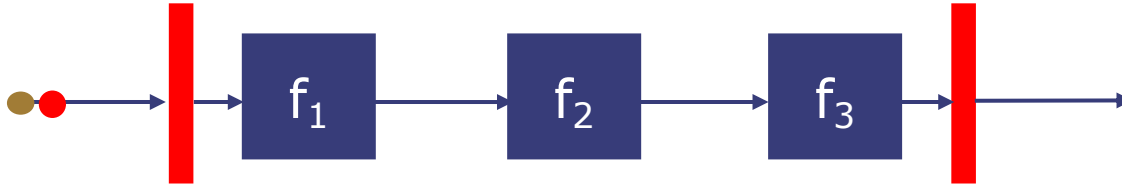
# Pipelining Design Alternatives


Several combinational modules in one pipeline stage (A)



One module per pipeline stage (B)

 

Folded reuse a block, multicycle (C)

 

Clock:  $B \approx C < A$

Area:  $C < A < B$

Throughput:  $C < A < B$

Good luck on the quiz!